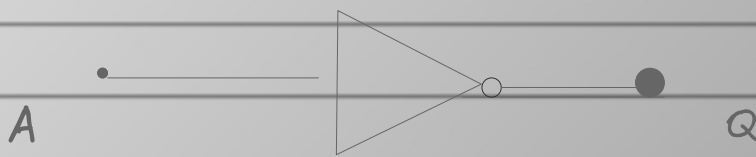


## Practical-1

Aim Study and verify the truth table of various logic gates (NOT, AND, OR, NAND, NOR, EX-OR, and EX-NOR).

### 1. NOT gate

#### Logic Diagram



#### Truth Table


A	Q
0	1
1	0

Boolean Expression  $Q = \text{not } A \text{ or } \overline{A}$

### 2. AND gate

#### Logic

## Diagram

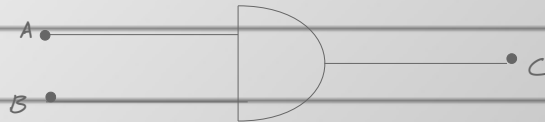

## Truth Table


A	B	Q
0	0	0
0	1	0
1	0	0
1	1	1

Boolean Expression  $Q = A.B$

## 3. OR gate

## Logic

Diagram

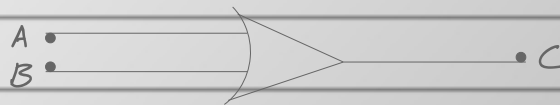


Truth Table

A	B	Q
0	0	0
0	1	1
1	0	1
1	1	1

4. NAND gate

Logic Diagram

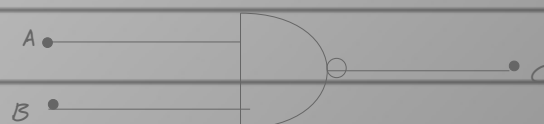

Truth

Table


A	B	Q
0	0	1
0	1	1
1	0	1
1	1	0

Boolean Expression

$$Q = A \cdot B$$

5. NOR gate

Logic Diagram

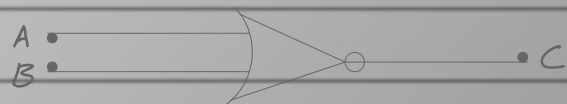

Truth Table

A	B	Q
0	0	


1		
0	1	0
1	0	0
1	1	0

Boolean Expression

$$Q = A + B$$

6. EX-OR gate

Logic Diagram

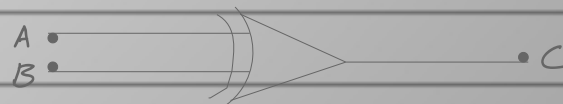

Truth Table

A	B	Q
0	0	0
0	1	1
1	0	1
1	1	

0

Boolean Expression

$$Q = A \oplus B$$

7. EX-NOR gate

Logic Diagram



Truth Table

A	B	Q
0	0	1
0	1	0
1	0	0
1	1	1

Boolean