

Practical-3

Design and verify a half full adder.

Aim : To design and construct half adder, full adder, circuits and verify the truth table using logic gates.

Theory :

HALF ADDER :

A half adder has two inputs for the two bits to be added and two outputs one from the sum 's' and other from the carry 'c' into the higher adder position. Above circuit is called as a carry signal from the addition of the less significant bit sum from the X-OR Gate the carry out from the AND gate.

FULL ADDER :

A full adder is a combinational circuit that forms the arithmetic sum of input; it consists of three input and outputs. A full adder is

useful to add three bits at a time but a half adder cannot do so. In full adder sum output will be taken from X-OR gate, carry output will be taken from OR Gate.

Logic Diagram :

Half Adder



Truth table :


Truth Table

A	B	Carry	Sum
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	

0

Full Adder

fulladder using two halfadder

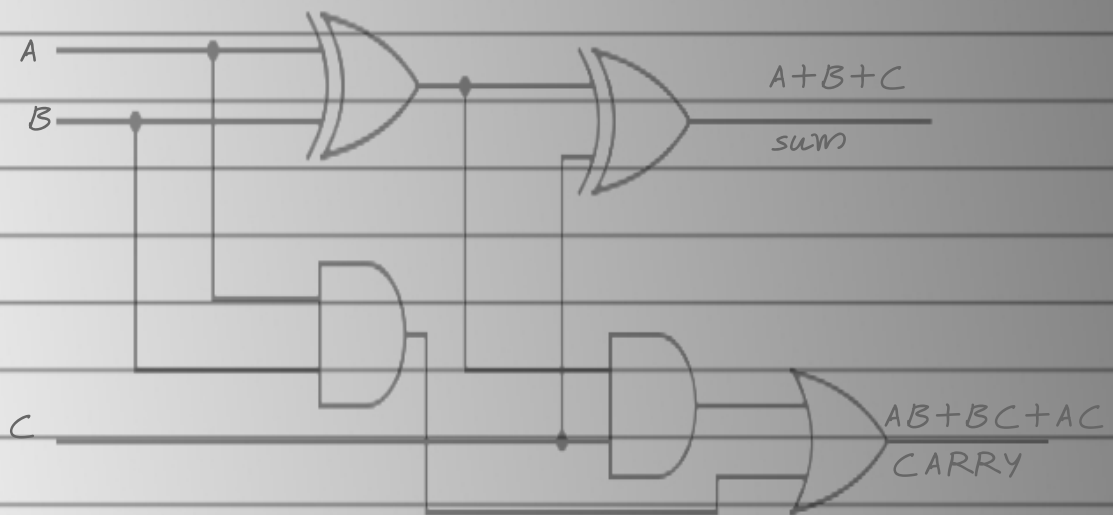

Truth table

A	B	C	Carry	Sum
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	